

Lab 6


10/10/2022


TA: You Zhou

Single layer neuron cell

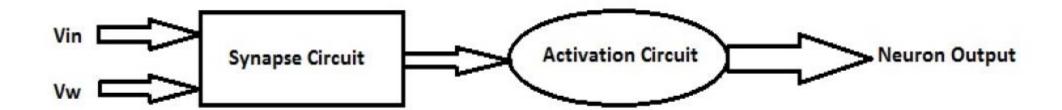

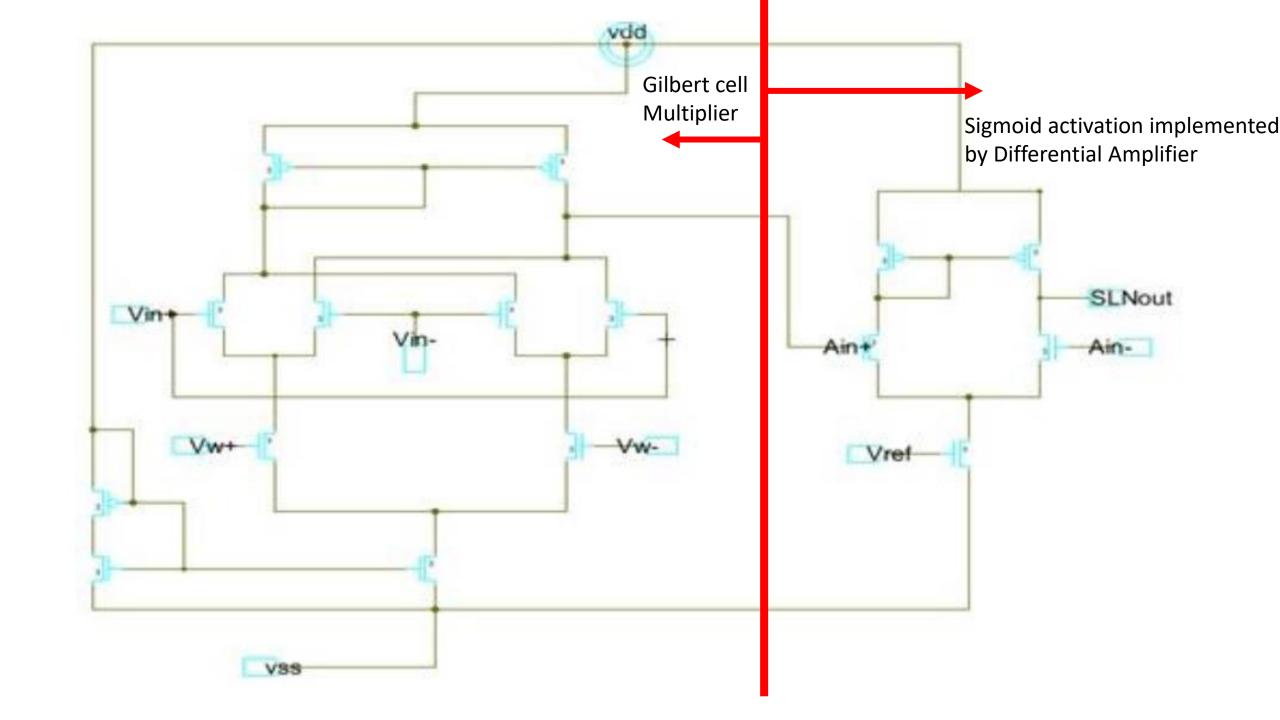

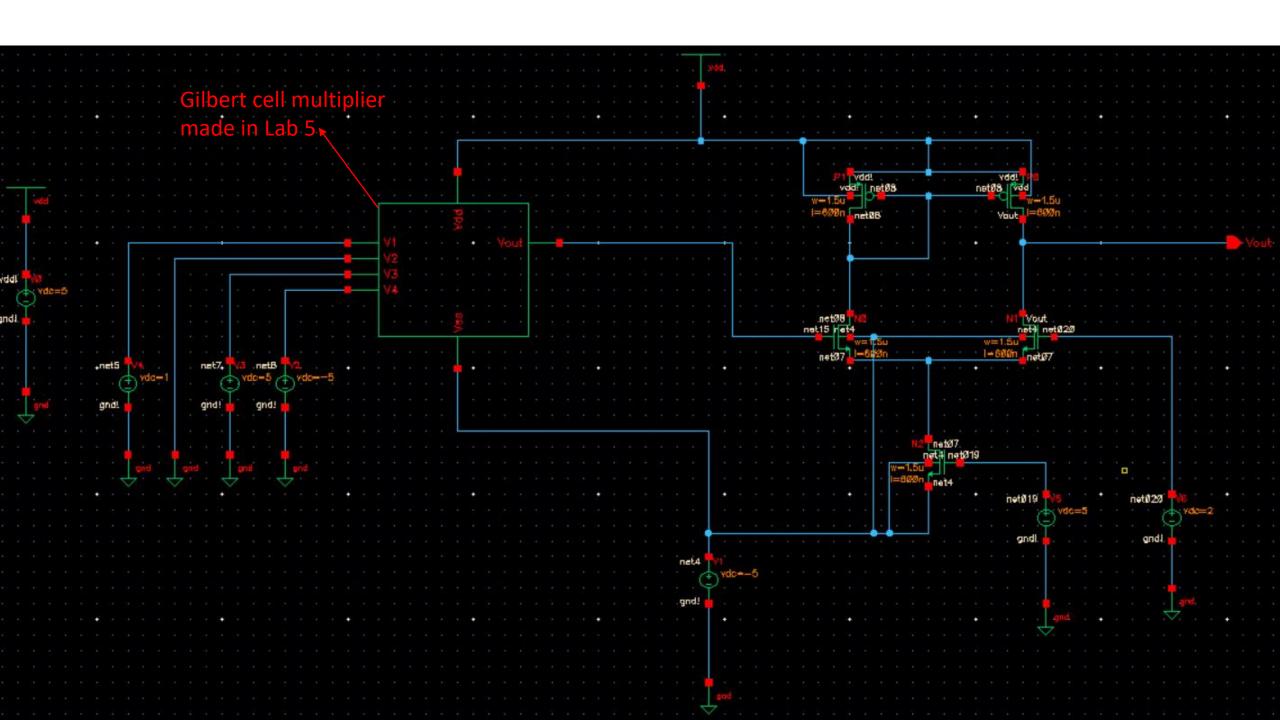

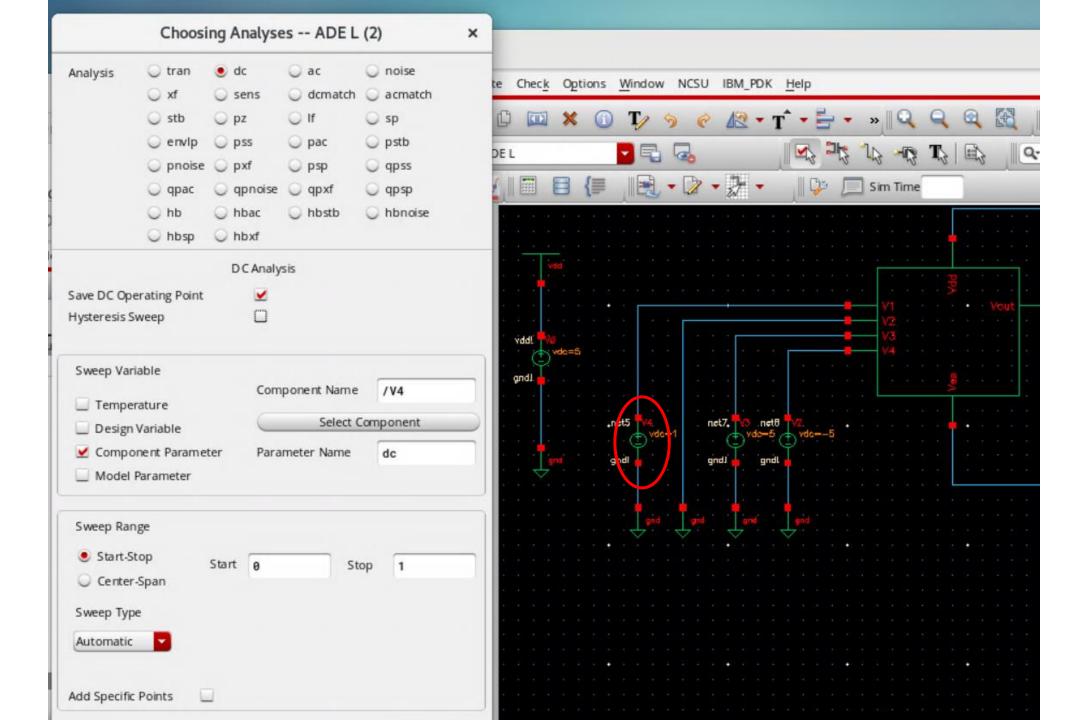

Select the input voltage, Gilbert multiplier output, Differential Amplifier output to be plotted

